


P116B Homework 4

Due 2/28/2020

1. In class, we discussed the concept of “data sparsification”. Imagine we have a system with 50,000 channels, each with 8 bits of data. We have two options for storing this data
 - Store all the data we read out, regardless of the signal size.
 - Only store channels that exceed a predefined threshold, along with their address.
 - (a) How many bits do I need to allocate for the address?
 - (b) At what “occupancy” (percentage of channels exceeding threshold) does it take less space to store all the data (with no addresses) rather than the “sparsified” version?
2. For the following module

```
module hw4 (  
    input clk,           // system clock  
    input D,  
    output reg Q0=0,  
    output reg Q1=0,  
    output reg Q2=0);    // Serial data bit  
  
    always @(posedge clk) begin  
        Q0 <= D;          // non-blocking statements  
        Q1 <= Q0|D;  
        Q2 <= Q0&Q1;  
    end  
  
endmodule
```

 Complete the following time line, assuming $Q1$, $Q2$ and $Q3$ all start at 0, and the D input is synchronous.




3. Repeat the previous problem if the non-blocking statements are replaced with blocking statements.

```
module hw4 (
    input clk,           // system clock
    input D,
    output reg Q0=0,
    output reg Q1=0,
    output reg Q2=0);    // Serial data bit


    always @(posedge clk) begin
        Q0 = D;           // blocking statements
        Q1 = Q0|D;
        Q2 = Q0&Q1;
    end

endmodule
```

 

 4. Redo the “parallel to serial converter” problem from a previous homework set, using Verilog code rather than discrete components.

As a reminder, this is a circuit that will load a four bit word ($A[3 : 0]$) in response to a “LOAD” signal, and then clock the bits out serially to Q over the next four clock cycles. The circuit should also issue a DATA output concurrent with the first serial data bit, to signal the start of serial data, as illustrated in the timeline below



As before, you may assume that the A_n bits are valid for at least one cycle, and the LOAD bit is synchronously asserted for exactly one clock cycle. Define your module as

```
module p2s (
    input clk,           // system clock
```

```
input [3:0] A,      // Input parallel word
input LOAD,        // synchronous load command
output reg DATA=0, // Serial data coming out
output reg Q=0);   // Serial data bit
```

You will simulate your design in the next problem.

5. Use EDA Playground to simulate the module you wrote in the previous problem. Once you create a profile account in EDA Playground
 - Under “Tools & Simulations”, select “Icarus Verilog 0.9.7”.
 - Select the “Open **EPWave** after run” radio button.
 - Give your project a unique name in the title bar of the window at the bottom.

Load your p2s module in the design.sv window, and download the file “ps2_testbench.v” from the “Files/FPGA Files” directory at the Canvas site and copy it into the testbench.sv window.

Save your project and click “Run”. Once you have things working, submit a screen shot of the output waveforms.